

试题名称:

电子线路

- 一、
1. (a) NPN 管 V_{BE} 反偏, $\therefore$ 截止
 - (b) PNP 管发射结正偏, 集电结反偏, $\therefore$ 放大区
 - (c) 集电结零偏, $\therefore$ 临界饱和
 - (d) $V_{BE}=0$ $I_B \neq 0$ $I_C \neq 0$ 证明发射结已短路, 损坏

2. ① $A_v = (-100) \times (-100) \frac{R_i}{R_o + R_i} = 3333.3$

② $A_v = \frac{R_i}{R_i + R_s} (-100) \frac{R_i}{R_o + R_i} (-100) \frac{R_L}{R_L + R_o} = 1190.5$

3. 由 $V_o = A_1 \times 10 \text{ mV} = 5.5 \text{ V} \rightarrow A_1 = 550$

$V_o = A_2 \times 15 \text{ mV} = -6.75 \text{ V} \rightarrow A_2 = -450$

$\left. \begin{array}{l} A_1 = 550 \\ A_2 = -450 \end{array} \right\} \rightarrow \begin{array}{l} A_c = A_1 + A_2 = 100 \\ A_d = A_1 - A_2 = 1000 \end{array}$

$\therefore \text{CMRR} = \frac{|A_d|}{|A_c|} = 10 \text{ or } 20 \text{ dB}$